

# COL215 Hardware Assignment 3b: AES Decryption

**Vanshika (2023CS10746)**  
**Laksh Goel (2023CS10848)**

November 10, 2024

## 1 Task

1. Combine Dedicated units to perform various round operations. Like multiplexer, gate array and Multiplier block for GF(28 ) (MAC): to perform element-wise multiplication to get one output value , into single control unit , and perform the round 10 times.
2. Control the read/write from the memories into the ports of control unit.

## 2 Design Decisions and Third level abstraction modules

### 2.1 InvMixColumns

We implemented the module for multiplication of one 8-bit entry of matrix with another 8-bit entry. For this, we divided multiplying into three operations, namely shift by one , shift by two and shift by three.

Shift by one shifts the entry by one value left and takes XOR with 0x1B if highest bit is on. Further shift two uses two instances of shift one to perform shift two, similarly shift three used three instances of shift one to perform shift three.

Inside multiplier module, we perform all three shifts to get three signals. Further, we take xor of whichever three signals out of these are required.

### 2.2 InvRowShift

After InvMixColumns operation, we are required to rotate elements in a row from right to left. Number of elements to be rotated depends on the row number, as shown in the figure.

We used 4X1 multiplexer for this operation. A 32-bit row and Row number was sent as input, which decides which select vector will be sent to multiplexers. Four multiplexers were required for this purpose, one for each element of a row.

## 2.3 InvSubbytes

In this, each element is replaced by a value determined using the INV\_SBOX matrix, which is stored in ROM as a 256-element vector, each a hexadecimal value.

Input of this code segment is an 8-bit hexadecimal value, which is sent as address to ROM, which then gives required value at output.

## 2.4 XOR operation

We implemented two XOR modules.

The first one takes two 8 bit hexadecimal and simply XOR them with each other.

Another XOR module takes input as two 128-bit hexadecimal strings and XOR 8-bits at a time, using the clock and assigns the final XOR to a result signal after all the 16 8-bit XOR are computed.

## 2.5 RAM controller

For reading and writing memory into ram we made a separate module. This module, is an fsm design where there are read , write and wait states. From the initial state according to write enable we move to write state or read state , and after each 8 bit write or read we wait for two wait states. This module using fsm returns me 4 vectors of 32 bit each .

## 2.6 ROM controller

For reading from ROM we have a separate module which reads from rom 8 bits at a time using fsm (READ and WAIT states ) and returns 4 vectors of 32 bit each.

# 3 second level abstraction modules

## 3.1 Four\_row

This module is for shifting the rows of matrix. We send 4 row vector of 32 bit each in this module and using abstraction from part 1 we shift all rows and send new 4 row vectors to my fsm controller.

## 3.2 Four\_sub

This module takes 4 vectors of 32 bit each and uses abstraction of inverse sub\_box from hardware 1 to make new 4 vectors of 32 bit each.

## 3.3 Four\_mult

This module takes 4 row vectors and performs multiplication using abstraction from the first part of the assignment and then returns 4 vectors of 32 bit each.

---

### 3.4 New\_design

In this module we use 4 vectors of 32 bit each and using clock after every 1 second we change the display segment to be displayed and send it to the display plain text module from assignment 2 .

## 4 Top level of abstraction

### 4.1 FSM controller

This has an FSM which performs the above task and decrypts the cipher text using the sequence of operations performed given using various states and WAITS .

## 5 Displaying the plain text

We did the following abstraction :

1. One module for converting input 8-bit hexadecimal into it's corresponding binary of 4-bit using ASCII codes.
  2. Another module for seven-segment single display from hardware 2
  3. Another module for 4 displays from hardware 2
  4. Another module that combines all these. It determines scrolling of one character within some constantxclock period time. Then takes 4 displays which are required to displayed at that time. Converts them to 4-bit using the first module. Then sends this to 4 display which further uses seven-segment single display to get cathodes for each character.
-

## 6 Simulations

### 6.1 FINAL OUTPUT ACCORDING TO ROW MAJOR, FOR SOME INPUT

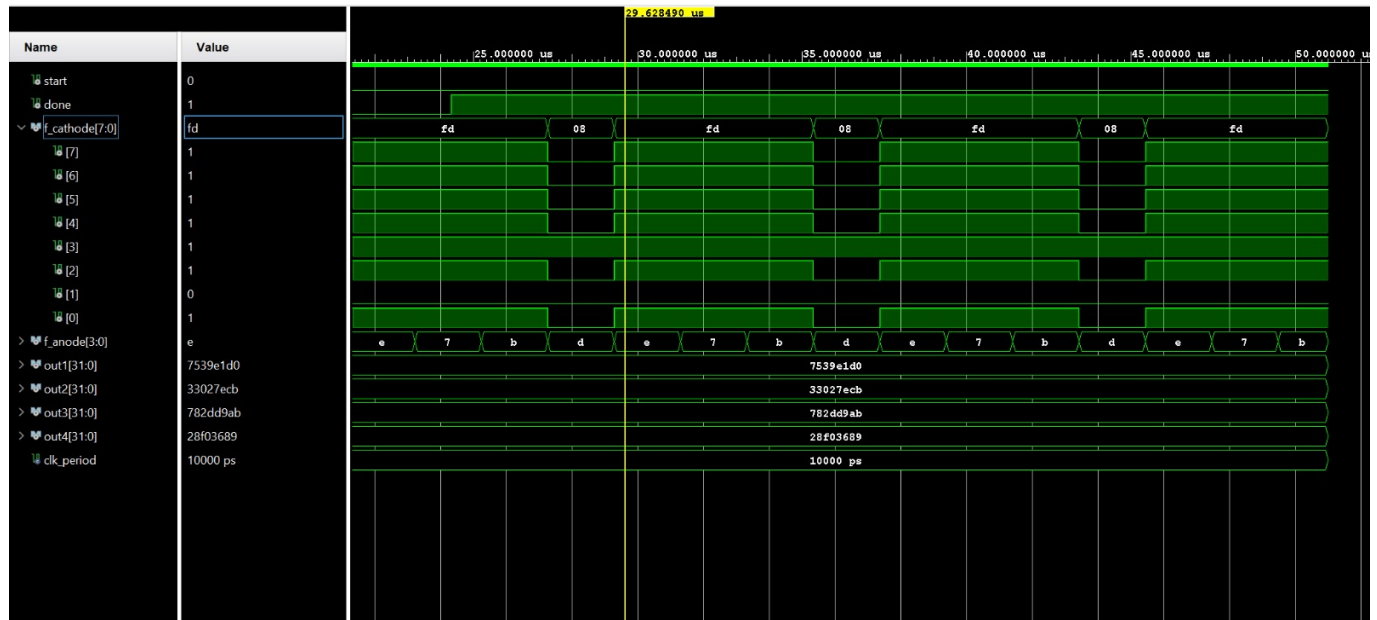


Figure 1: simulation

## 6.2 Inv. sub of whole matrix

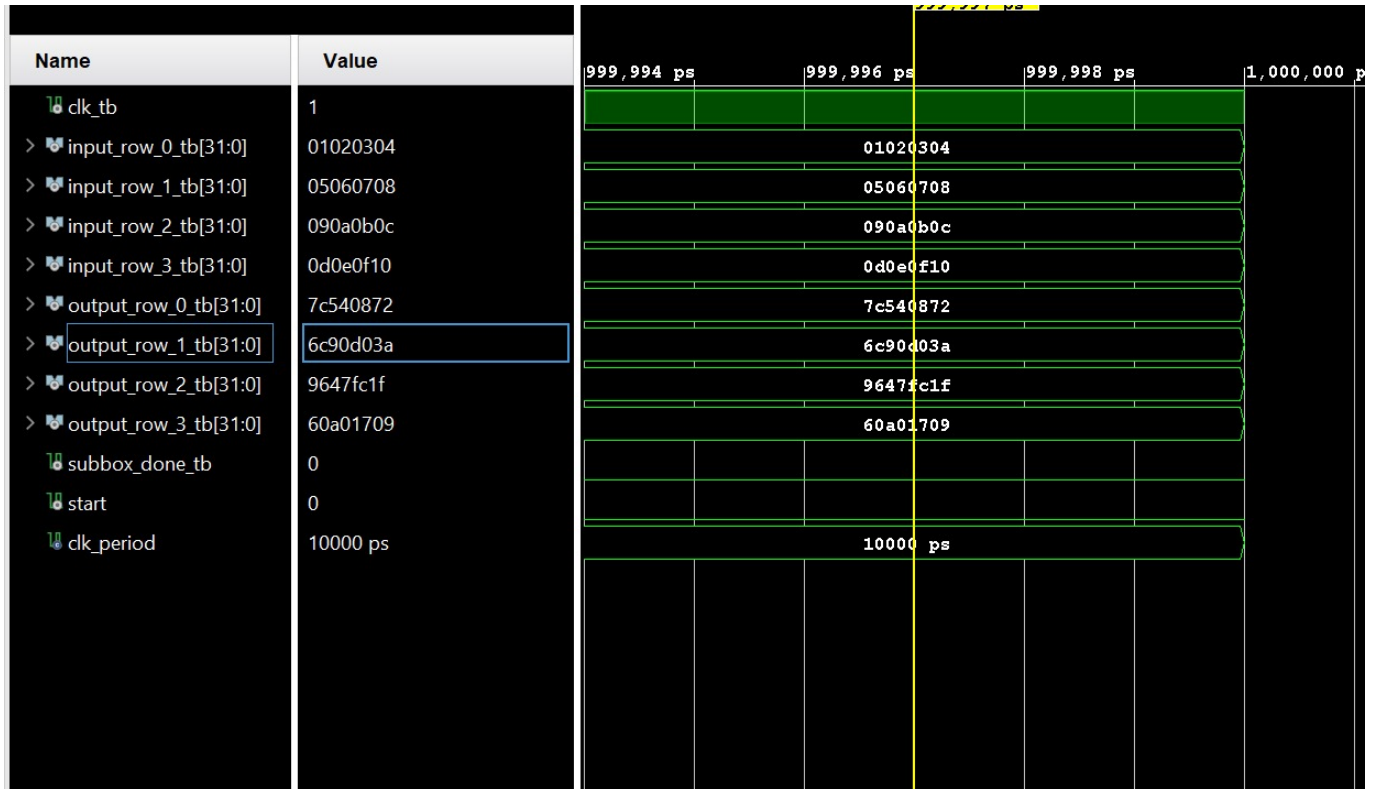


Figure 2: simulation

6.3 whole row shift

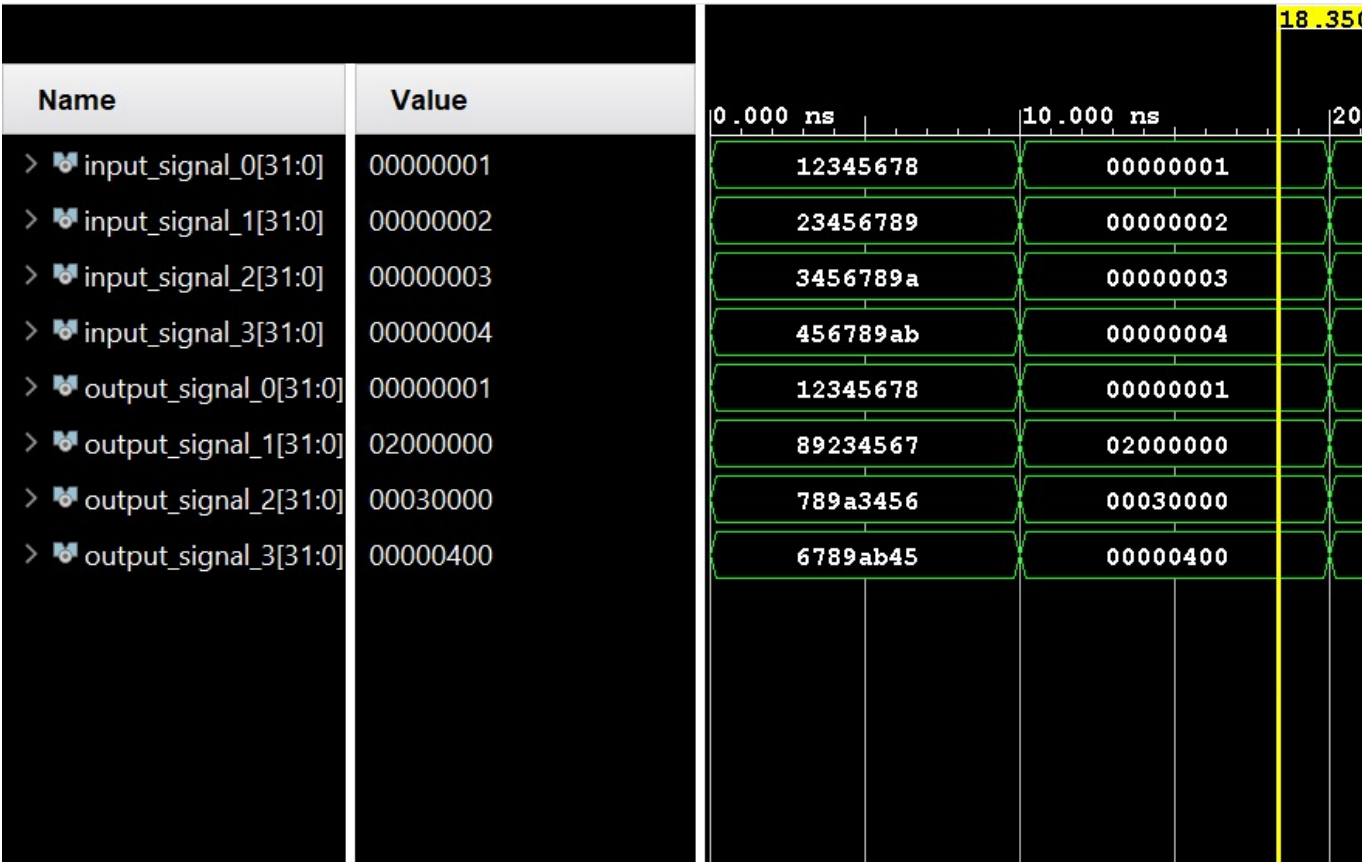


Figure 3: simulation

6.4 XOR simulation

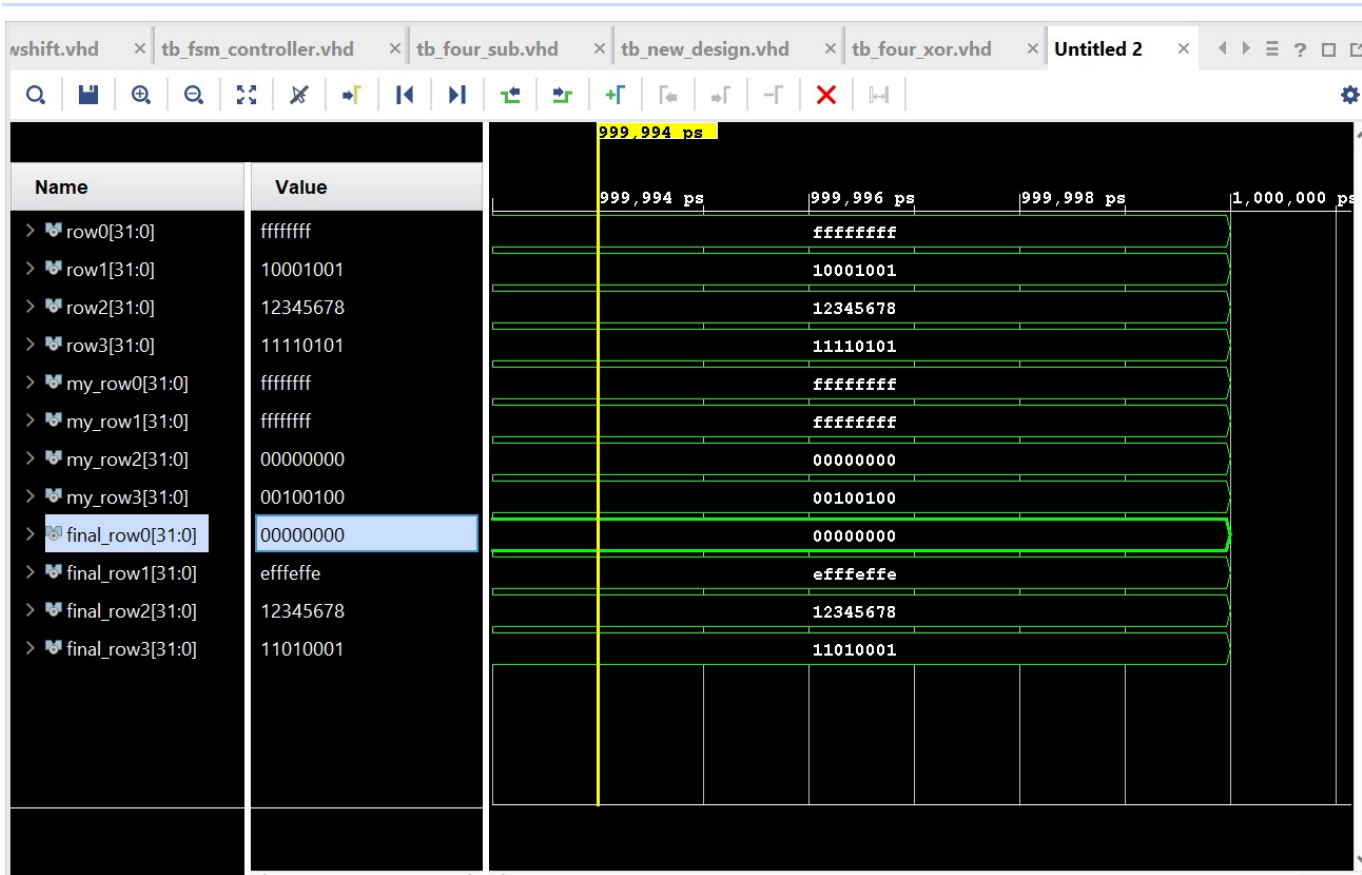


Figure 4: simulation

6.5 DISPLAY AND SCROLLING SHOWN



Figure 5: simulation

6.6 whole matrix multiplication (inv mix columns)

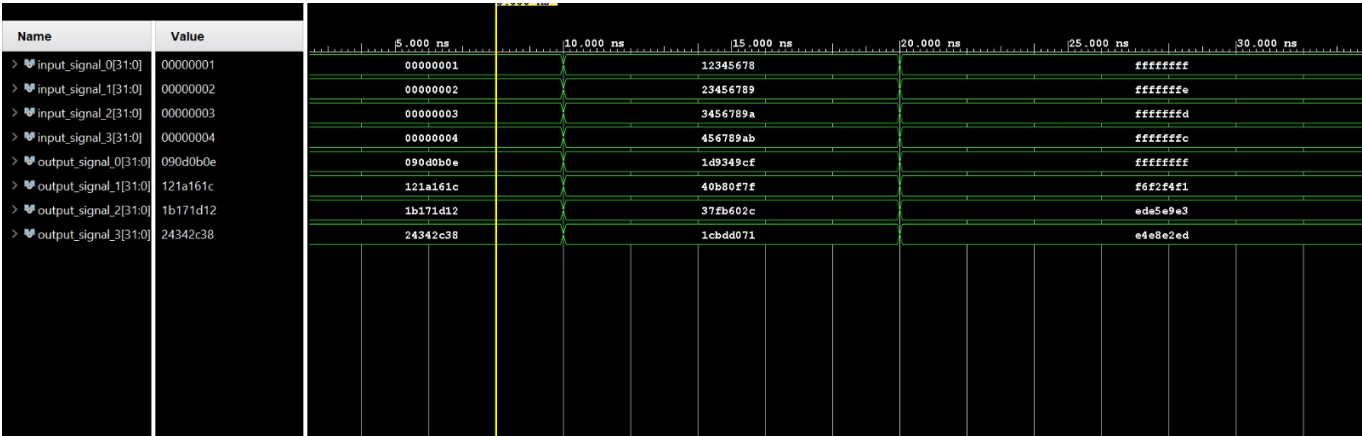


Figure 6: simulation

7 Resource utilization

Constraints	Status	WNS	TNS	WHS	THS	WBSS	TPWS	Total Power	Failed Routes	Methodology	RQA Score	QoR Suggestions	LUT	FF	BRAM	URAM	DSP
constrs_1	synth_design Complete!												1292	2612	0	0	0

Figure 7: resource1

its	Status	WNS	TNS	WHS	THS	WBSS	TPWS	Total Power	Failed Routes	Methodology	RQA Score	QoR Suggestions	LUT	FF	BRAM	URAM	DSP	Start	Elapsed	Rur
1	synth_design Complete!												1292	2612	0	0	0	11/11/24, 12:53 AM	00:00:43	Viv

Figure 8: resource2



## 8 Schematic

### 8.1 FSM

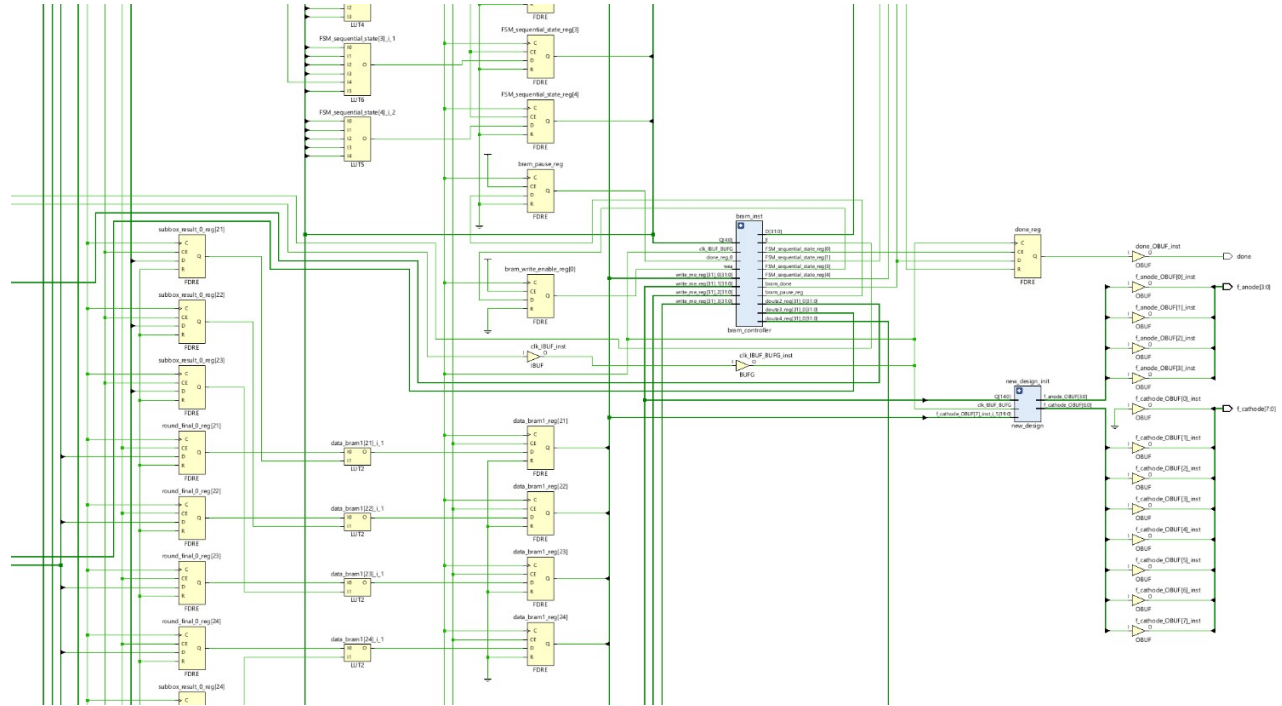


Figure 9: FSM schematic 1

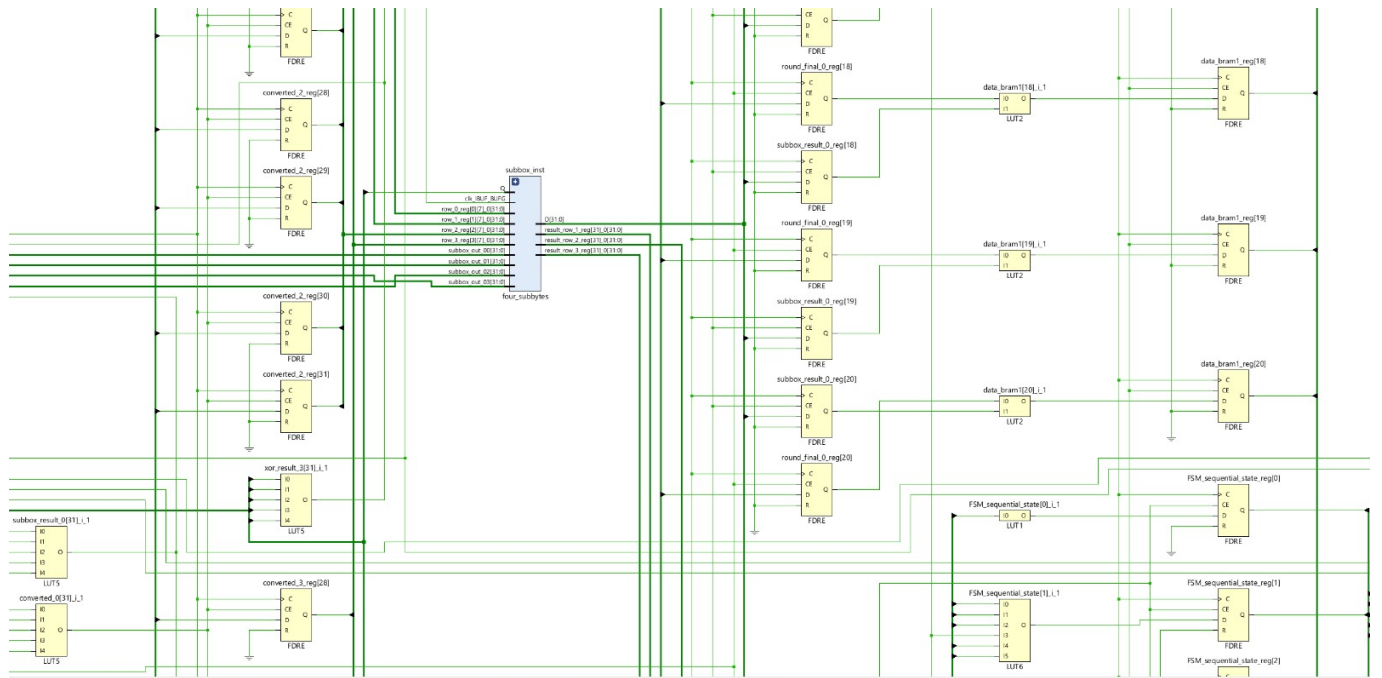


Figure 10: FSM schematic 2

 


Figure 11: FSM schematic 3

## 9 Block diagram

### 9.1 whole matrix multiplication (inv mix columns)

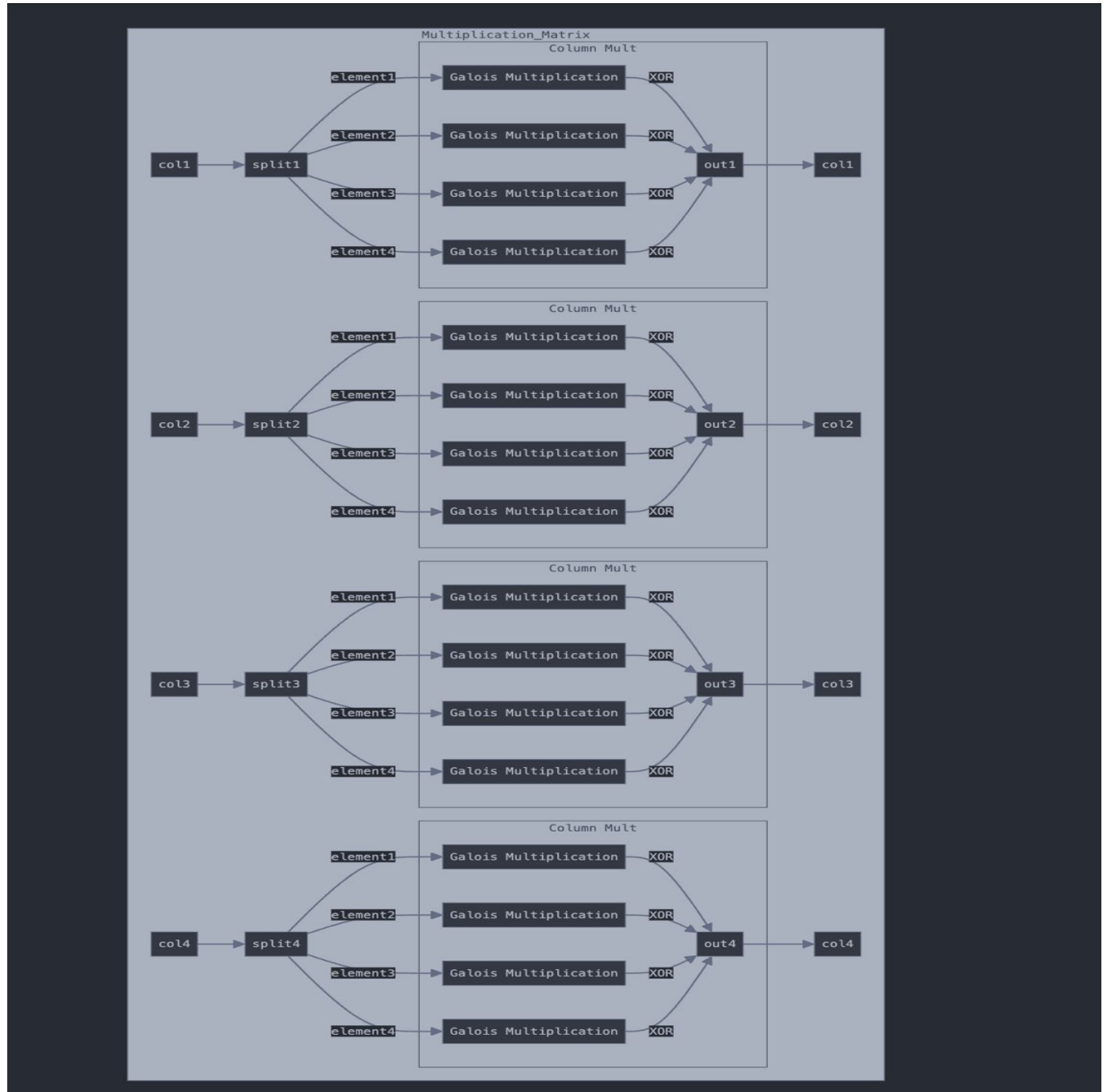


Figure 12: block diagram

## 9.2 Inv. sub of whole matrix

 


Figure 13: block diagram

### 9.3 whole row shift

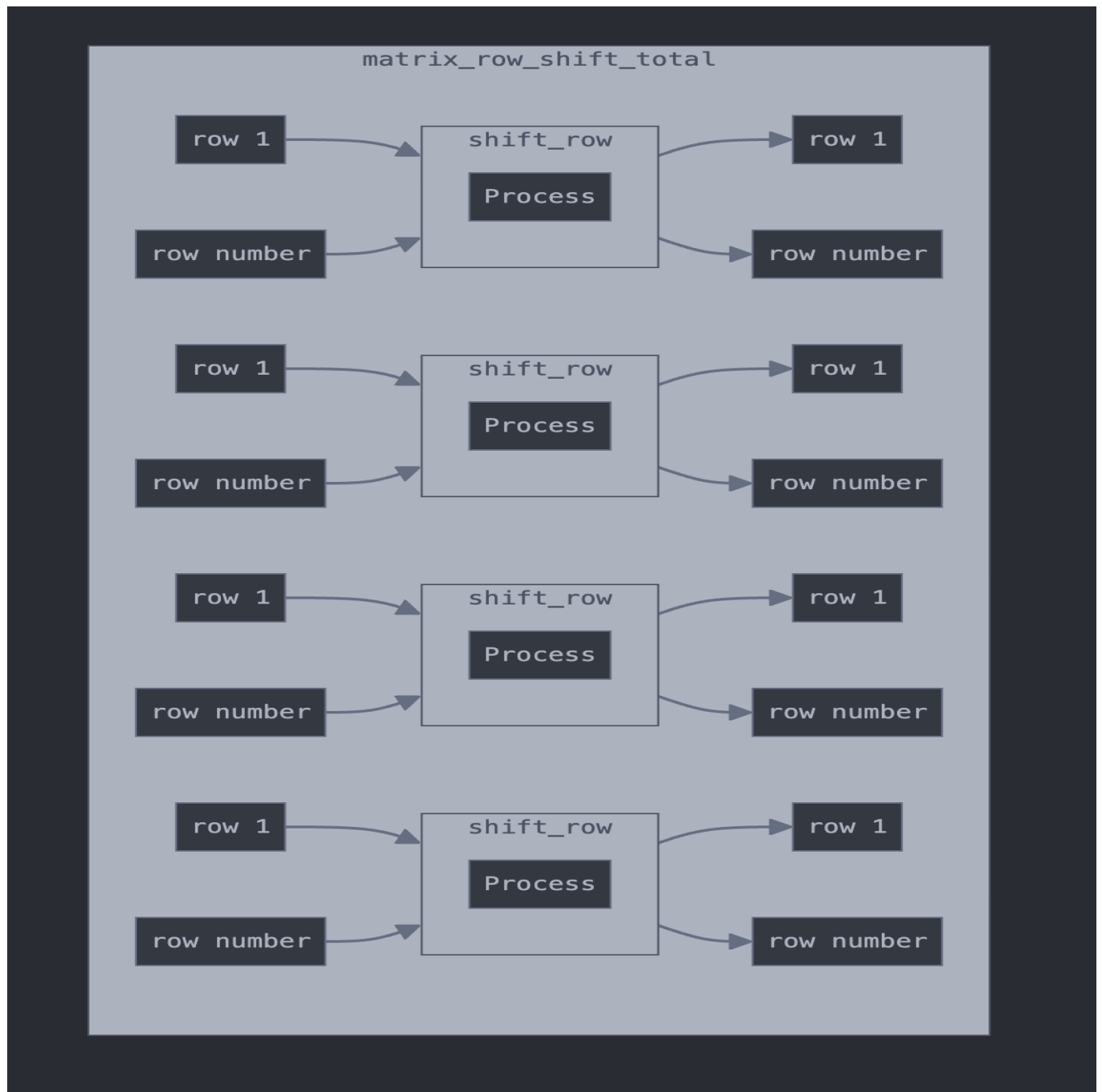


Figure 14: block diagram

## 9.4 XOR

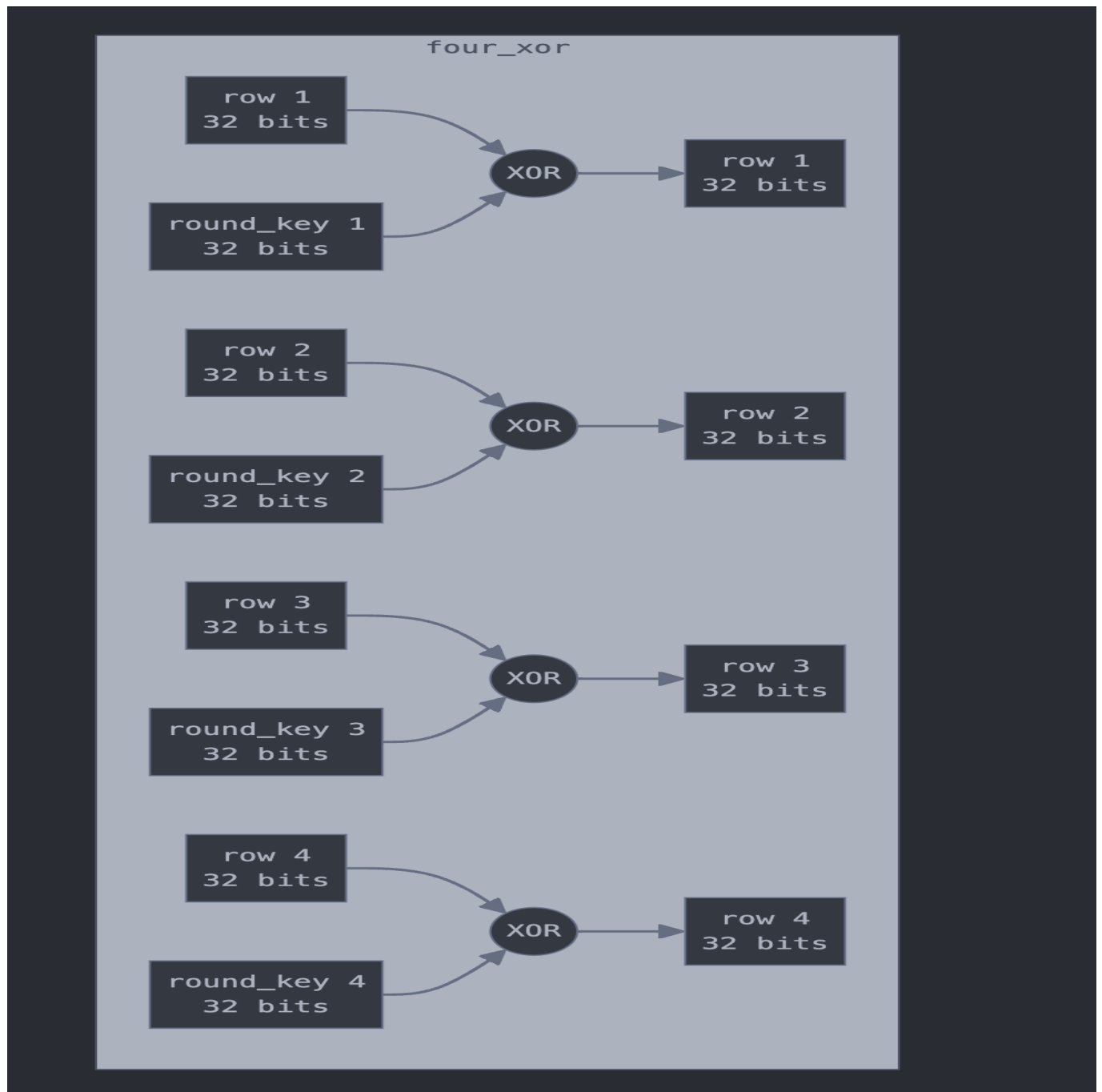


Figure 15: block diagram

## 9.5 FSM

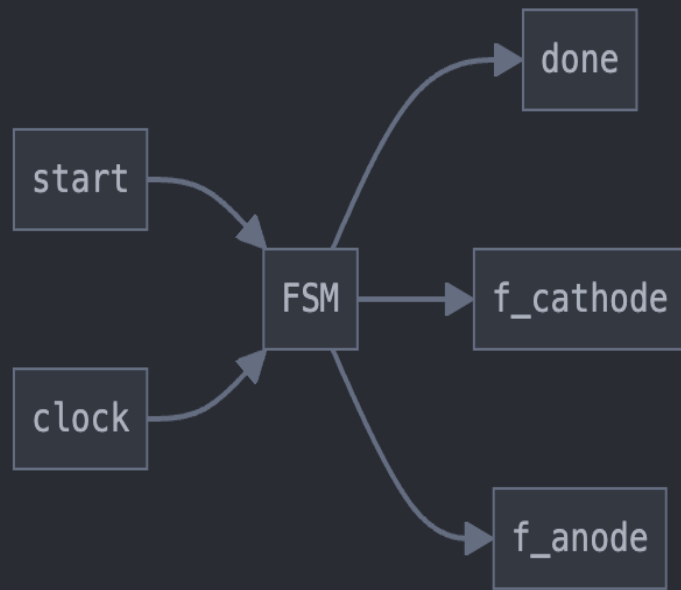


Figure 16: block diagram



## 10 simulation depicting the change of states in final fsm

NOTE: STATE 1 = READ

STATE 2 = XOR

STATE 3= MULTIPLY

STATE 4 = INVERSE ROW SHIFT

STATE 5 = INVERSE SUB BYTES

STATE 6 = WRITE

STATE 7 = PAUSE(DONE)



Figure 17: starts from 5 , goes to 2 , 3, 4 again 5

 


Figure 18: goes to state 1, then 2 , then 4 then 5

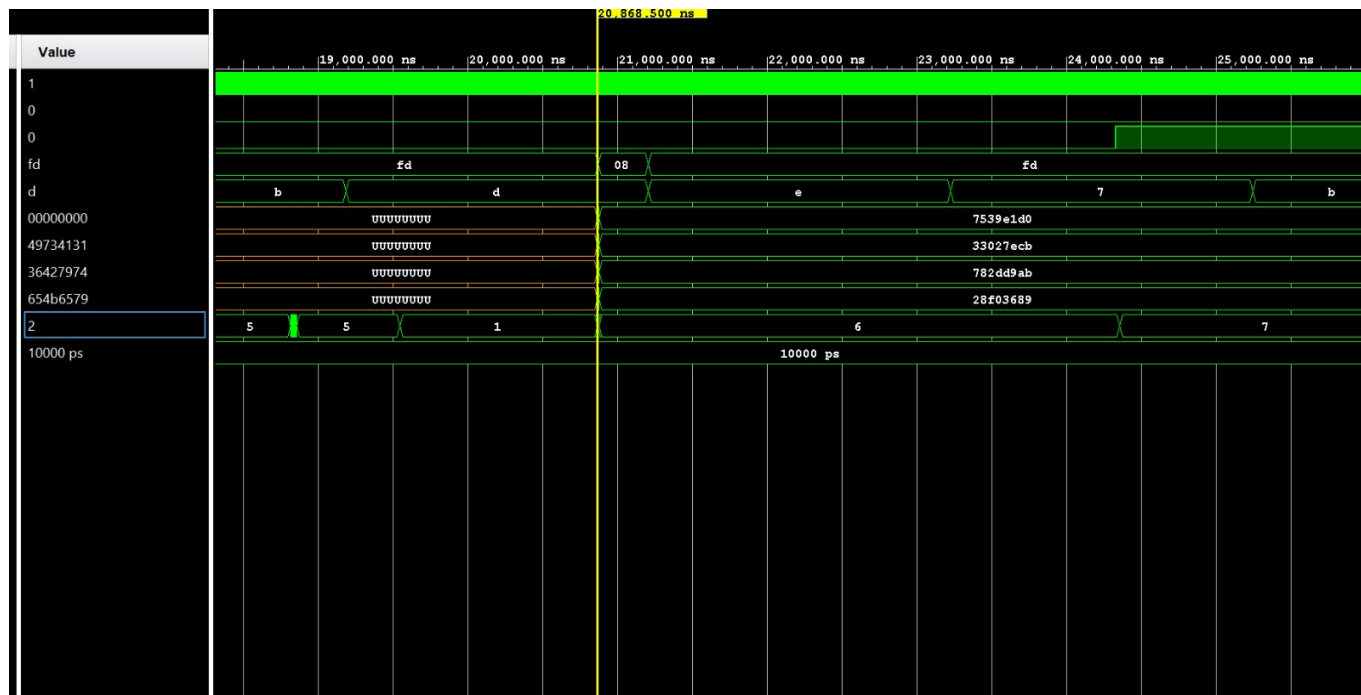


Figure 19: there are rounds, 5 to 5 then 5 to 5 and so on, after that it does reading(state 1) then the cursor marks the point 2 which final XOR and then final writing state 6 and then pause which is state 7

## 11 STATE TRANSITION DIAGRAM OF FSM

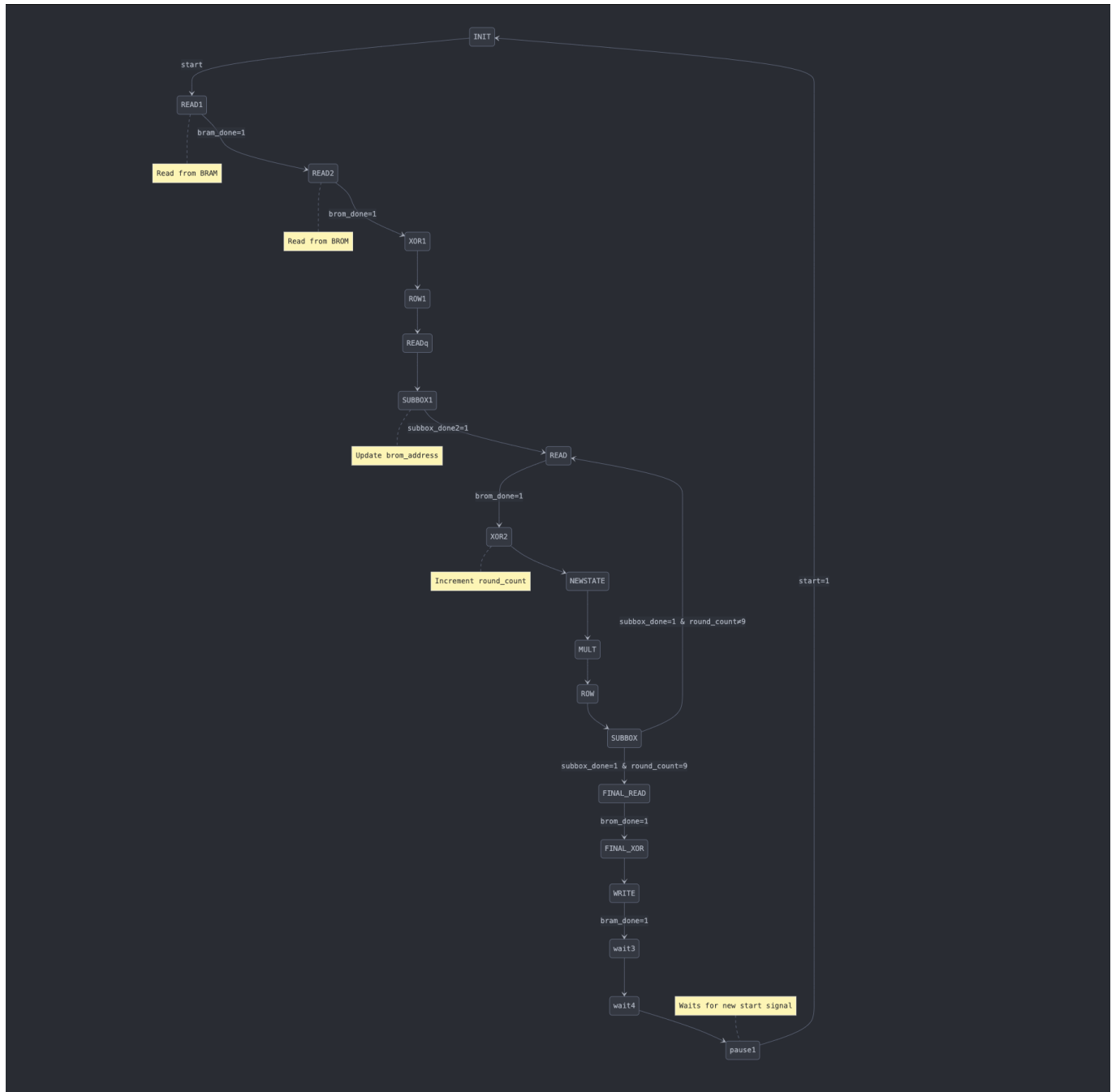


Figure 20: state transition diagram